

# Microelectronic Circuits

## 8<sup>th</sup> Edition


A. Sedra, K.C. Smith  
T. Chan Carusone, V. Gaudet

*Spice Problems Solutions*  
*Chapter 4*


*Prepared by: Nijwm Wary*  
*2019*

**Problem: 4.56**

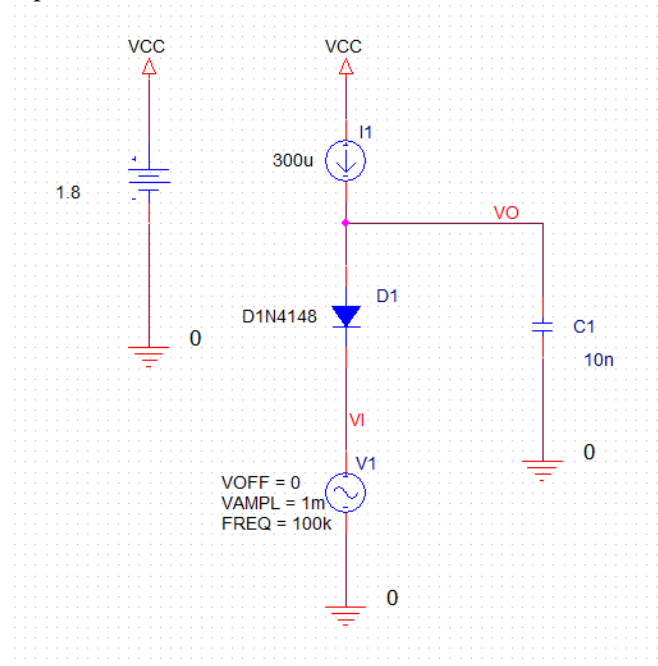1. The schematic for this problem is shown below



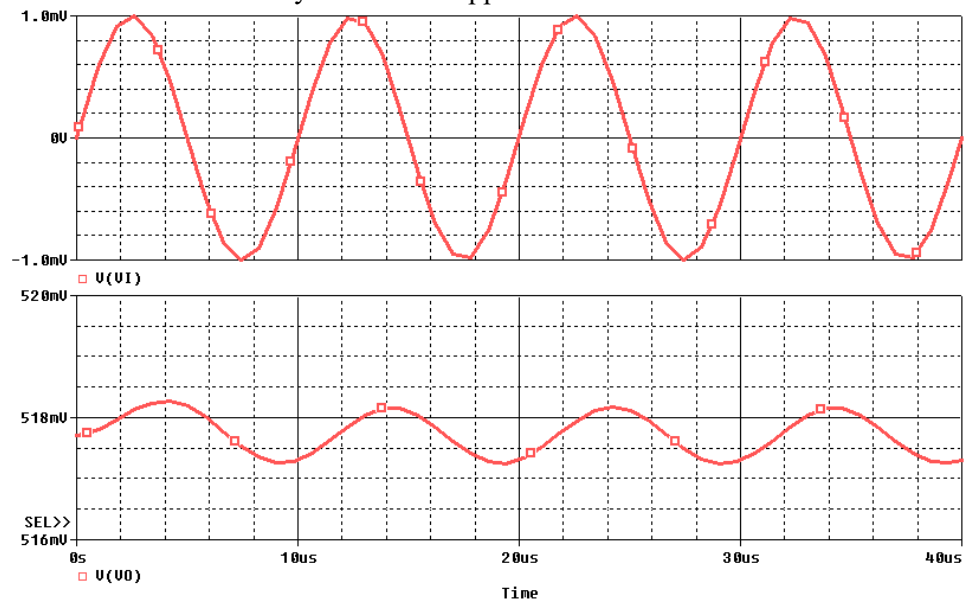2. Run the netlist and perform the transient analysis. Plot  $V(VI)$  and  $V(VO)$ . For  $-45$  degree phase shift the waveform should shift by  $1.25 \mu\text{s}$ . It happens when  $I=160 \mu\text{A}$ .



3. Using similar simulations, find the phase shift for  $I=16 \mu\text{A}$  and  $I=1.6 \text{ mA}$ .

**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Problem: P4_56 *****
***** Main circuit begins here*****
D1      VO VI D1N4148
V1      VI 0
+SIN 0 1m 100k 0 0 0
V_sup   VCC 0 1.8
C1      0 VO 10n
I1      VCC VO DC 300u
***** Main circuit ends here *****


***** Model of D1N4148 begins here*****
.model D1N4148 D(Is=2.682n N=1.836 Rs=.5664 Ikf=44.17m Xti=3 Eg=1.11 Cjo=4p
+          M=.3333 Vj=.5 Fc=.5 Isr=1.565n Nr=2 Bv=100 Ibv=100u Tt=11.54n)
***** Model of D1N4148 ends here*****

***** Analysis begins here*****
.TRAN 0.01uS 40uS
*.STEP LIN PARAM AMPL 1 3 0.5
.PROBE
.END
***** Analysis ends here*****


```

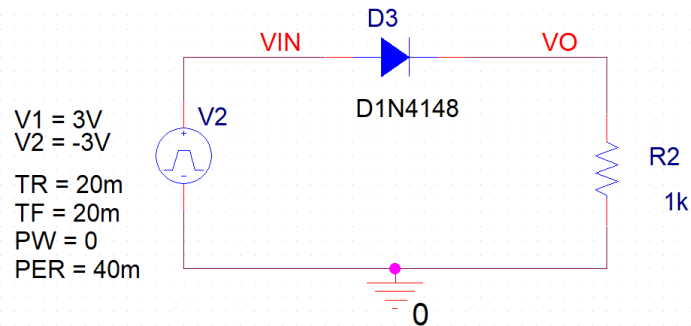**Problem: 4.67**

- The schematic for this problem is shown below



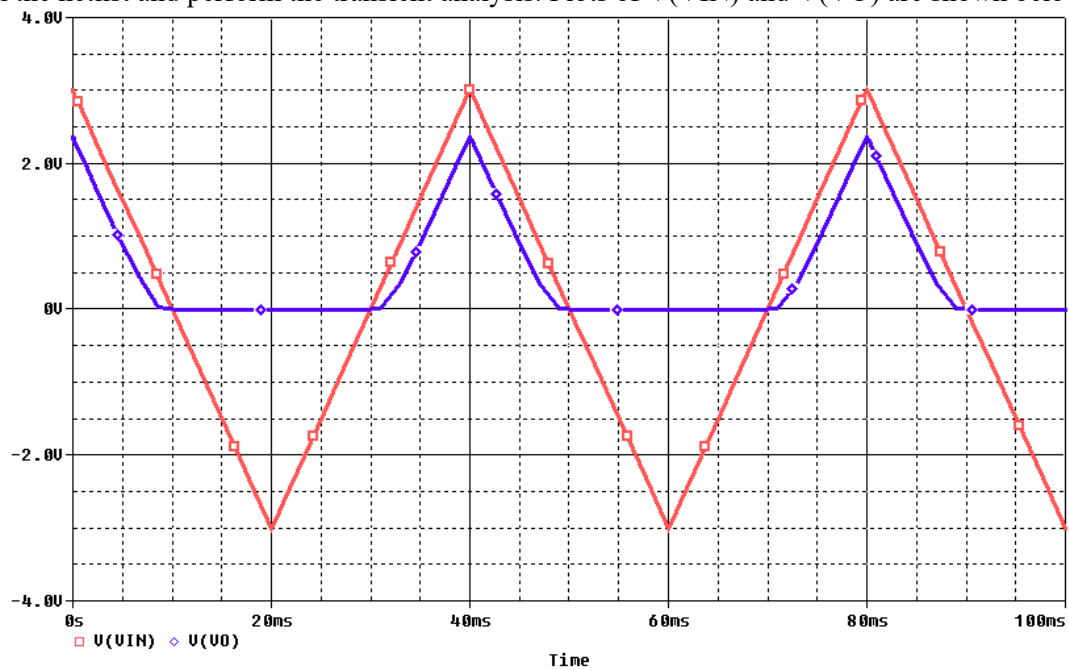- Run the netlist and perform the transient analysis. Plots of  $V(VIN)$  and  $V(VO)$  are shown below.



- Calculate the average of  $VO$  by using the trace expression  $YatLastX(AVG(V(VO)))$  (this expression is valid only in PSpice. Enter this expression by selecting Trace->Evaluate Measurement). It is 504.6 mV

**Netlist:**

Copy the netlist given below and paste it into a text file and save it with \*.cir extension.

```

*****Problem: P4_67 *****
***** Main circuit begins here*****

D_D3      VIN VO D1N4148
R_R2      0 VO 1k
V_V2      VIN 0
+PULSE 3V -3V 0 20m 20m 0 40m
***** Main circuit ends here *****

***** Model of D1N4148 begins here*****
.model D1N4148 D(Is=2.682n N=1.836 Rs=.5664 Ikf=44.17m Xti=3 Eg=1.11 Cjo=4p
+           M=.3333 Vj=.5 Fc=.5 Isr=1.565n Nr=2 Bv=100 Ibv=100u Tt=11.54n)
***** Model of D1N4148 ends here*****

***** Analysis begins here*****
.TRAN 0.01mS 100mS
.PROBE
.END
***** Analysis ends here*****

```